

Electricity and circuit – GCSE Physics

CONTENTS:

1. Introduction
2. What is an Electrical Circuit?
3. What are series and parallel circuits?
4. What is potential difference, current, and resistance?
5. What is Ohm's Law?
6. How are Charge, Current, and Time Related?
7. How are Energy, Voltage, and Charge Related?
8. Solving questions with circuit diagrams
9. Solved examples
10. FAQs

1. Introduction

- An **Electrical circuit** is a closed path that allows electric current to flow through it.
- It connects electrical components using conductors to perform a specific function using electricity.
- Electrical circuits make it possible to control and distribute electrical energy safely and efficiently.

Where it is used:



Home Appliances



Electronics




Transportation

Electricity and circuit – GCSE Physics

2. What is an Electrical Circuit?

- An **Electrical circuit** is a closed loop path that allows electric current to flow, allowing energy to power devices and systems.
- It connects some components so that electricity can do useful work.
- Without electrical circuits, we could not use electricity to light our homes, charge devices, run machines, or operate communication systems.



Basic Electric circuit:

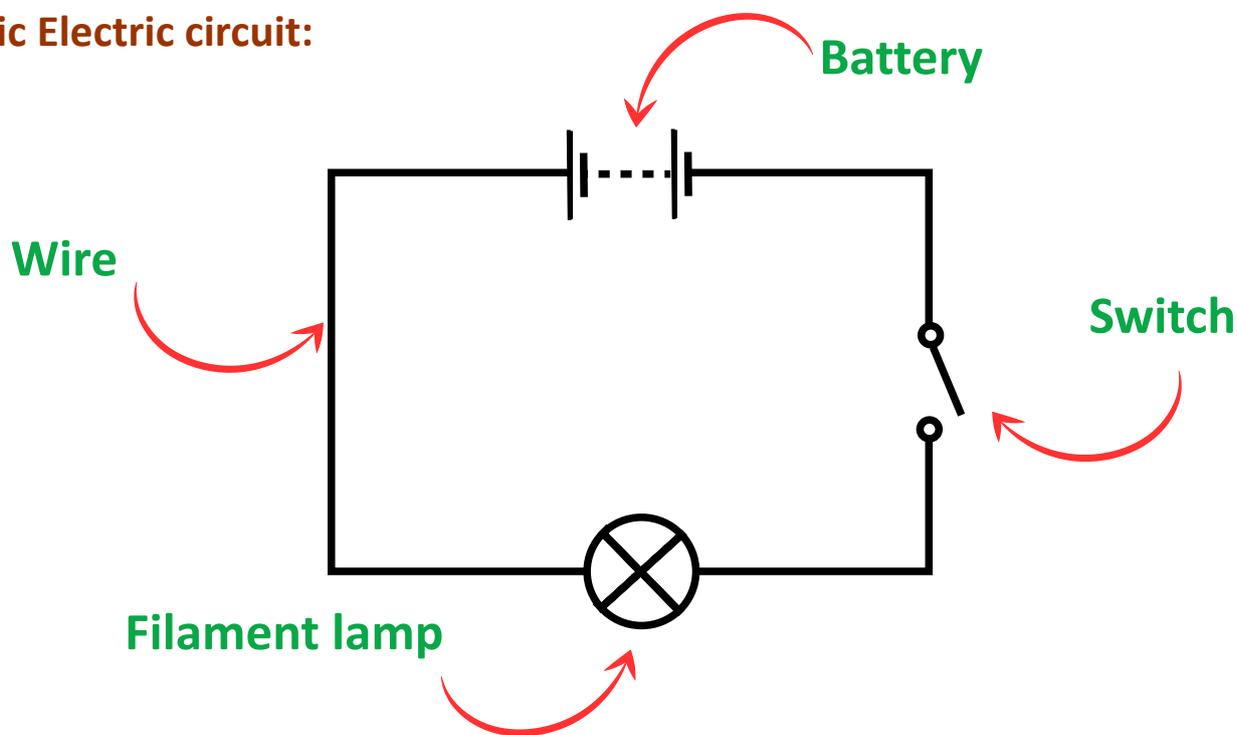

Components used in an electrical circuit with their symbols:

Components	Use	Symbol
Cell	To provide electric power	
Battery	To supply more electrical power.	

Electricity and circuit – GCSE Physics

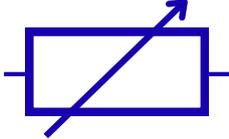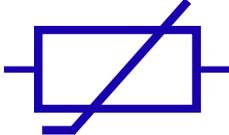
Components	Use	Symbol
Switch	Control the flow of electricity.	 Closed switch  Open switch
Filament Lamp (Bulb)	To convert electrical energy into light energy.	
Diode	To control the direction of current in a circuit.	
Ammeter	To monitor the amount of current flowing through the circuit.	
Voltmeter	To check the voltage supplied or dropped across circuit components.	
Fixed Resistor	To control the current in a circuit to a fixed value.	
Variable Resistor	To change the current in a circuit as needed.	
Thermistor	To detect to temperature changes in a circuit	

Electricity and circuit – GCSE Physics

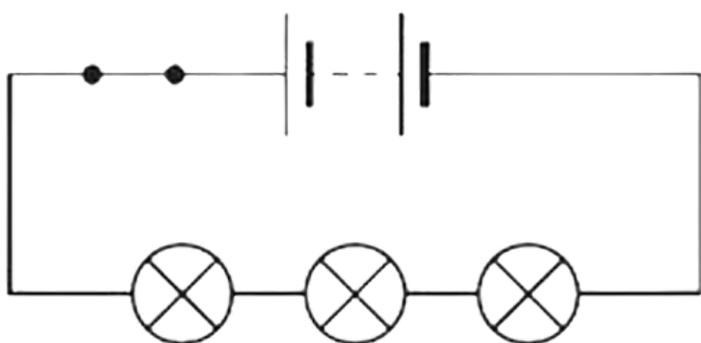3. What are series and parallel circuits?

Series Circuit:

- In **Series circuit**, the components are connected end-to-end in a single path, so the same current flows through all of them.
- **Example:** A simple flashlight with two batteries.



Total Potential Difference


$$V_{\text{total}} = V_1 + V_2 + V_3 + \dots$$

Total Current

$$I_{\text{total}} = I_1 = I_2 = I_3 = \dots$$

Parallel Circuit:

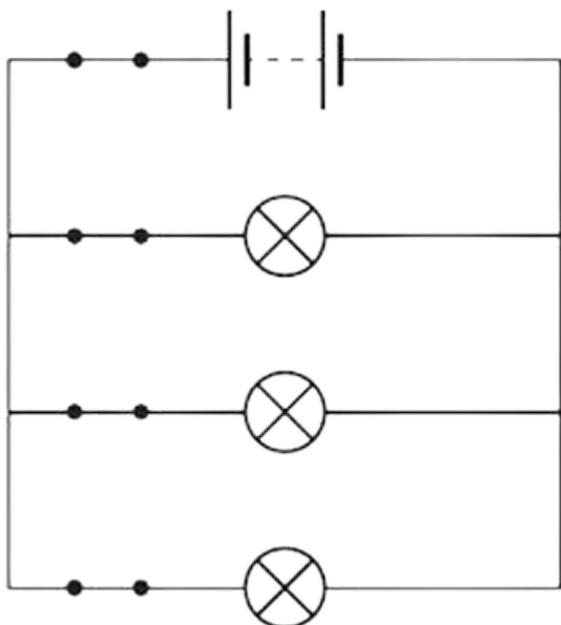- In **Parallel circuit**, the components are connected across multiple paths, so voltage is the same across each branch, but current can vary.
- **Example:** Home appliances (lights, fans, etc.) wired separately to the mains.



Total Potential Difference

$$V_{\text{total}} = V_1 = V_2 = V_3 = \dots$$

Total Current

$$I_{\text{total}} = I_1 + I_2 + I_3 + \dots$$

Electricity and circuit – GCSE Physics

4. What is potential difference, current, and resistance?

Potential difference:

- **Definition:** The force required for the flow of electrons in a circuit is called potential difference.
- **Unit:** Volts (**V**)
- **Provided by:** A cell or battery.

Current:

- **Definition:** The flow of electric charge (usually electrons) through a conductor is called current.
- **Unit:** Amperes (**A**)
- **Provided by:** A cell or battery pushing charges through the circuit.

Potential difference:

- **Definition:** The property of a material that opposes the flow of electric current.
- **Unit:** Ohms(**Ω**)
- **Provided by:** Resistors and the materials of wires/components in the circuit.

5. What is Ohm's Law?

- **Ohm's Law** states that the current through a conductor is directly proportional to the potential difference across it, if the temperature remains constant.
- It is written as:

$$V = I \times R$$

Electricity and circuit – GCSE Physics

Where:

- **V** = Potential difference
- **I** = Current
- **R** = Resistance

Example: If a circuit has a current of 3 A and a resistance of 3 Ω , find the voltage across it.

Solution:

Given:

- **A** = 3A
- **R** = 3 Ω

Using formula:

$$V = I \times R$$

Plug the values:

$$V = 3A \times 3\Omega$$

$$V = 9V$$

Therefore, the voltage across the circuit is **9 V**.

Electricity and circuit – GCSE Physics

6. How are Charge, Current, and Time Related?

⚡ Charge ⚡

- **Definition:** A measure of the **total current** that flowed within a certain period of **time**. It is carried by particles like electrons and protons.
- **Symbol:** Q or q
- **Unit:** Coulomb (C)

How to Calculate Charge:

Formula:

$$Q = I \times t$$

Where:

- **Q** = Charge
- **I** = Current
- **t** = Time

Example: A current of **5 A** flows through a circuit for **6 seconds**. Calculate the charge that flows through the circuit.

Solution:

Given:

- **A** = 5A
- **t** = 6s

Using formula:

$$Q = I \times t$$

Plug the values:

$$Q = 5A \times 6s$$

$$Q = 30 C$$

Electricity and circuit – GCSE Physics

7. How are Energy, Voltage, and Charge Related?

Energy

- **Definition:** In electricity, energy is the work done when charge moves through a voltage.
- **Symbol:** E
- **Unit:** Joule (J)

How to Calculate Charge:

Formula:

$$E = V \times Q$$

Where:

- Q = Charge
- E = Energy
- V = Voltage

Example: A charge of **15 C** moves through a voltage of **9 V**. Calculate the energy transferred.

Solution:

Given:

- Q = 15C
- V = 9V

Using formula:

$$E = V \times Q$$

Plug the values:

$$E = 9V \times 15C$$

$$E = 135 J$$

Therefore, **135 joules** of energy are transferred.

Electricity and circuit – GCSE Physics

8. Solving questions with circuit diagrams


Steps to solve question with circuit diagram

Step#1: Identify given values in the circuit.

Step#2: Choose the correct formula.

Step#3: Substitute values and calculate the unknown.

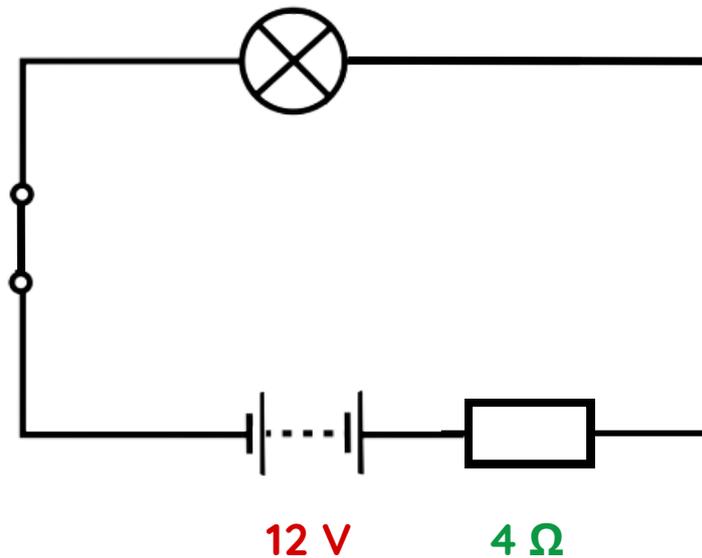Example: A circuit has a 12 V battery and a 4 Ω resistor in series. Find the current.



Solution:

Step#1: Identify given values in the circuit.

Given:

- $V = 12 \text{ V}$
- $R = 4 \Omega$

Step#2: Choose the correct formula.

Using Ohm's Law:

$$V = I \times R \quad \text{or} \quad I = \frac{V}{R}$$

Electricity and circuit – GCSE Physics

Step#3: Substitute values and calculate the unknown.

Substitute the values:

$$I = \frac{12V}{4\Omega}$$


$$I = 3 \text{ A}$$

Therefore, the current flowing in the circuit is 3 A.

9. Solved Examples

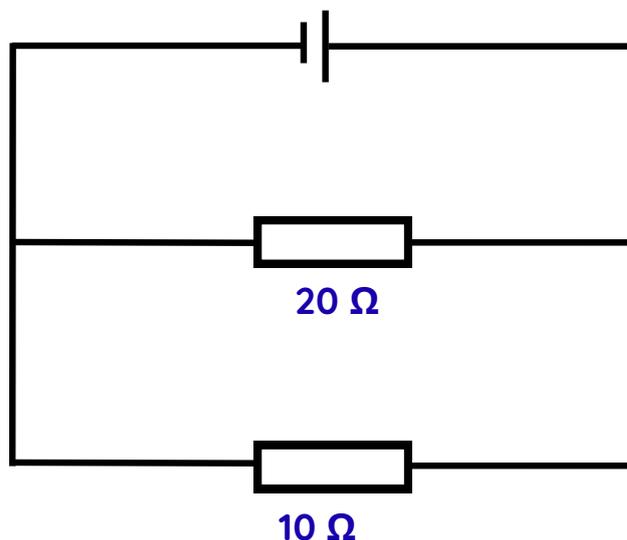Problem1: A parallel circuit has a 10 Ω resistor and a 20 Ω resistor. The current through the 20 Ω resistor is 0.6 A.

Calculate: 1. The current through the 10 Ω resistor, and
2. The total voltage of the cell.



Solution:

Step#1: Identify given values in the circuit.

- Given:**
- $R_1 = 10\Omega$
 - $R_2 = 20\Omega$
 - $I_2 = 0.6 \text{ A}$

Electricity and circuit – GCSE Physics

Step#2: Choose the correct formula.

In parallel circuits,

Voltage across each branch is the same:

$$V = I \times R$$

Step#3: Substitute and calculate.

- The voltage across the resistors:

Using,

$$V = I_2 \times R_2$$

$$V = 0.6A \times 20\Omega$$

$$V = 12V$$

The voltage across the 10 Ω resistor is also 12 V.

- The current through the 10 Ω resistor:

Using,

$$I_1 = \frac{V}{R_1}$$

$$I_1 = \frac{12V}{10\Omega}$$

$$I_1 = 1.2A$$

The current through the 10 Ω resistor is 1.2 A.

- The total current from the cell:

In parallel:

$$I_{\text{total}} = I_1 + I_2$$


Electricity and circuit – GCSE Physics

$$I_{\text{total}} = 1.2 \text{ A} + 0.6 \text{ A}$$

$$I_{\text{total}} = 1.8 \text{ A}$$

The total current from the cell is **1.8 A**.

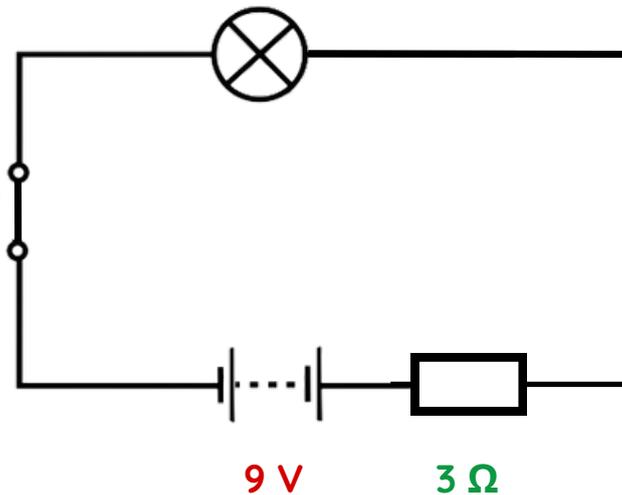Problem2: A battery of 9 V is connected in series with a 3 Ω resistor. Calculate the charge flowing through the circuit in 4 seconds.



Solution:

Step#1: Identify given values in the circuit.

Given:

- $V = 12 \text{ V}$
- $R = 4 \Omega$
- $t = 4 \text{ s}$

Step#2: Choose the correct formula.

To find charge (Q), use:

$$Q = I \times t$$

First, find current (I) using Ohm's Law:

Electricity and circuit – GCSE Physics

$$I = \frac{V}{R}$$

Step#3: Substitute and calculate.

- Find the current:

$$I = \frac{9V}{3\Omega}$$

$$I = 3 A$$

- Find the charge:

$$Q = I \times t$$

$$Q = 3A \times 4s$$

$$Q = 12C$$

The charge flowing through the circuit in 4 seconds is **12 C**.

Electricity and circuit – GCSE Physics

10. FAQs

1. What is an electric circuit?

It is a closed path that allows electric current to flow.

2. What does Ohm's Law state?

Ohm's Law states that:

$$V = I \times R$$

3. What is electric charge?

Electric charge is a property of particles like electrons and protons that causes them to experience a force in an electric field.

4. What is potential difference?

It is the work done to move unit charge between two points. Measured in volts (V) using a voltmeter.

5. What is resistance?

It is the opposition to the flow of electric current. Measured in ohms (Ω) using an ohmmeter.

6. What happens to current in a series circuit?

Current stays the same in all parts of the circuit. It has only one path to flow.

Total Potential Difference

$$V_{\text{total}} = V_1 + V_2 + V_3 + \dots$$

Total Current

$$I_{\text{total}} = I_1 = I_2 = I_3 = \dots$$